

Safia Reazi

170LC

Lab 5

5/26/2020

## SIM 1

*Value of  $R_d$*

- $R_d = (V_{dd} - V_{out})/I_d$ 
    - $R_d = (5V - 2.5V)/200 \mu A$
- $R_d = 12.5k\Omega$**

*Transistor width*


- $I_d = \frac{1}{2} \mu C_{ox}(W/L)(V_{gs} - V_t)^2$ 
    - $200 \mu A = \frac{1}{2} (0.6m)(W/L)(1.8V - 1.4V)^2$
    - $L = 2 \mu m$
    - $W/L = 4.16 \mu m$
- $W = 8.32 \mu m$**

*DC input voltage*

- $g_m = 2I_d/(V_{gs} - V_t) \Rightarrow V_{gs} - V_t = 2I_d/g_m \Rightarrow V_{gs} = 2I_d/g_m + V_t$ 
    - $g_m = 1mS, V_t = 1.4V$
    - $V_{gs} = 2(200 \mu A)/1mS + 1.4V$
- $V_{in} = V_{gs} = 1.8V$**

## SIM 2

## DC Operating Point Analysis

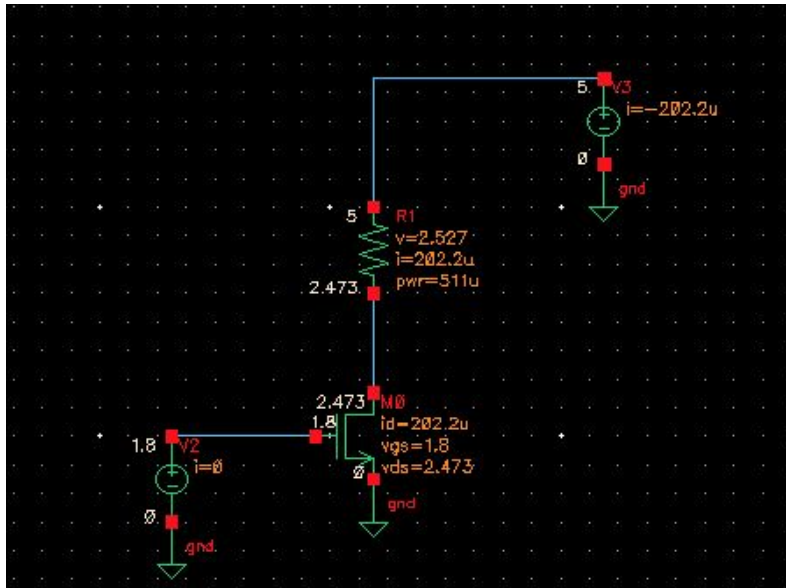


### Dominant pole of amplifier

- From the results window on Cadence:
    - $C_{bd} = 49.44\text{fF}$
    - $C_{bs}, C_{gd} = 0\text{F}$
    - $C_{gd} = 287.3\text{aF}$
    - $C_{gs} = 4.118\text{fF}$
  - $C_{gs}: \tau_1 = C_{gs} \cdot R_1 = 0$
  - $C_{bd}: \tau_2 = C_{bd} \cdot (r_o \parallel R_d)$
  - $C_{gd}: \tau_3 = C_{gd} \cdot (r_o \parallel R_d)$
  - $\tau(\text{total}) = \tau_1 + \tau_2 + \tau_3$ 
    - $(C_{bd} + C_{gd})(r_o \parallel R_d)$
  - Frequency Pole:  $f_{p1} = 1/2\pi \cdot \tau(\text{total}) = 1/2\pi [(C_{bd} + C_{gd})(r_o \parallel R_d)]$ 
    - $1/2\pi [(C_{bd} + C_{gd})(r_o \parallel R_d)]$
    - $r_o = 1/g_{ds} = 1/1.024 \mu\text{S} = 0.976\text{M}\Omega$
    - $r_o \parallel R_d = 1.23\text{e}4\Omega$
    - $1/2\pi [(49.44 + 0.28) \cdot 1\text{e-}15\text{F} \cdot (1.23\text{e}4\Omega)]$
- $f_{p1} = 250\text{MHz}$**

## SIM 3

### 3dB Frequency Point

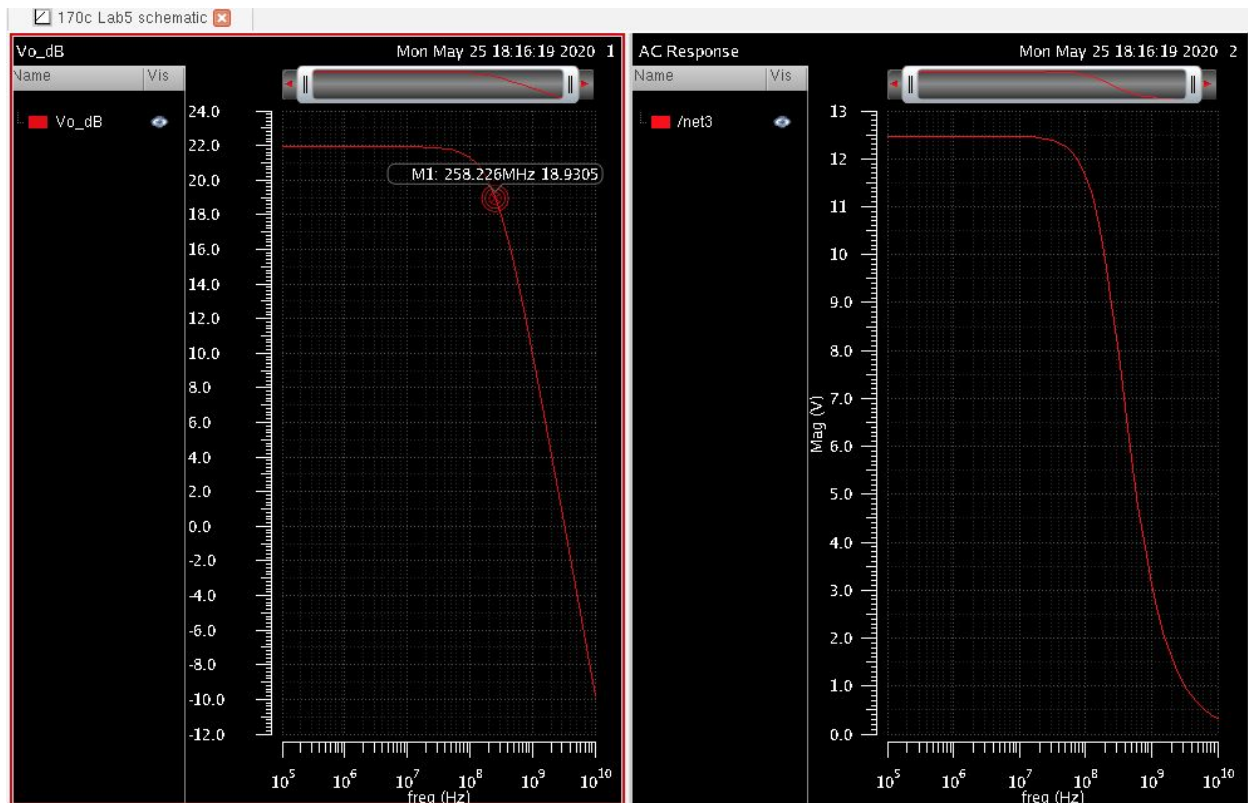

- Calculated frequency: 250MHz
- Simulation Frequency: 258MHz
- Percent Error: 3.1%

### SIM 4

#### Value of Rs

- $R_s = (V_{out} - V_s) / I_d$ 
  - $R_d = (2V - 0V) / 200 \mu A$
  - **$R_s = 10k\Omega$**

#### Transistor width


- $I_d = \frac{1}{2} \mu C_{ox} (W/L) (V_{gs} - V_t)^2$ 
  - $200 \mu A = \frac{1}{2} (0.6m) (W/L) (1.6V - 1.4V)^2$
  - $L = 2 \mu m$
  - $W/L = 16.6 \mu m$
  - **$W = 38 \mu m$**

### DC input voltage

- $g_m = 2I_d/(V_{gs}-V_t) \Rightarrow V_{gs} - V_t = 2I_d/g_m \Rightarrow V_{gs} = 2I_d/g_m + V_t$ 
  - $g_m = 2\text{mS}$ ,  $V_t = 1.4\text{V}$
  - $V_{gs} = 2(200\text{ }\mu\text{A})/2\text{mS} + 1.4\text{V} = 1.6\text{V}$
- **$V_{in} = V_{gs} + V_{out} = 1.6\text{V} + 2\text{V} = 3.6\text{V}$**

### SIM 5

#### DC Operating Point Analysis

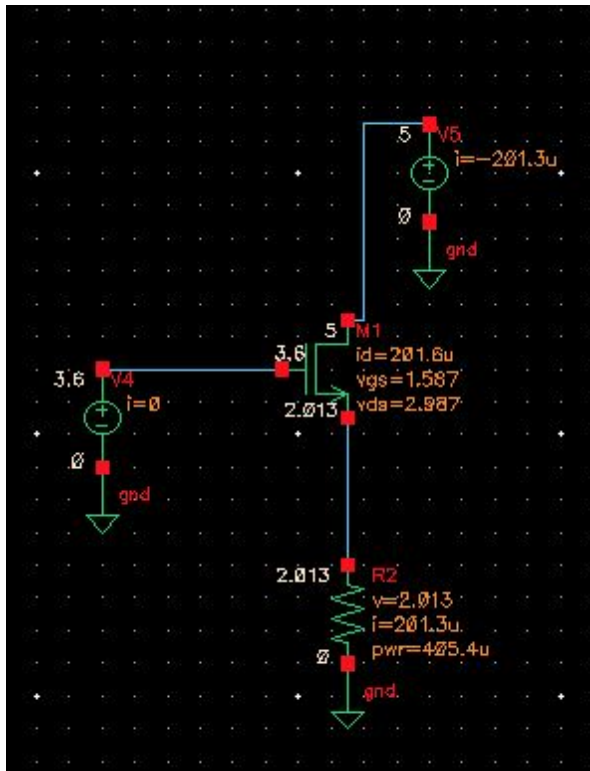


- From the results window on Cadence:
  - $C_{bd} = 37.14\text{fF}$
  - $C_{bs} = 53.33\text{fF}$
  - $C_{gd} = 1.312\text{fF}$
  - $C_{gs} = 18.81\text{fF}$
- $C_{gs}$ :  $\tau_1 = C_{gs} \cdot (R_s \parallel r_o \parallel 1/g_m)$
- $C_{bs}$ :  $\tau_2 = C_{bs} \cdot (R_s \parallel r_o \parallel 1/g_m)$
- $C_{gd}$ :  $\tau_3 = C_{gd} \cdot (R_{gd}) = 0$

- $\tau(\text{total}) = \tau_1 + \tau_2 + \tau_3$ 
    - $(C_{gs} + C_{bs})(R_s \parallel r_o \parallel 1/g_m)$
  - Frequency Pole:  $f_{p1} = 1/2\pi \cdot \tau(\text{total}) = 1/2\pi [C_{gs} + C_{bs}](R_s \parallel r_o \parallel 1/g_m)$ 
    - $1/2\pi [(C_{gs} + C_{bs})(R_s \parallel r_o \parallel 1/g_m)]$
    - $r_o = 1/g_{ds} = 1/1.023 \mu S = 0.976 M\Omega$
    - $g_m = 2mS \Rightarrow 1/g_m = 500\Omega$
    - $R_s \parallel r_o \parallel 1/g_m = 495\Omega$
    - $1/2\pi [(18.81 + 53.33) \cdot 1e-15 F \cdot (495\Omega)]$
- **$f_{p1} = 4.46GHz$**

## SIM 6

### 3dB Frequency Point

 

- Calculated frequency: 4.46GHz
- Simulation Frequency: 5.39GHz
- Percent Error: 17.2%

## Conclusion

In this simulation we were asked to design a common-drain and common-source CMOS amplifier. For the circuits we determined the resistor value, transistor width, and dc input voltage. The circuits were simulated with the design constraints and the calculated values were compared to the simulation results. The dominant pole was determined using the capacitor values given in Cadence. After the DC operating point analysis, an AC analysis was performed to calculate the 3dB frequency point and compare it with the estimated values. For the common-drain circuit there was a 3.1% error and for the common-source it was 17.2%.