

Safia Reazi

170LC

Lab 1


ID: 21415003

4/14/2020

Problem 1

A.


V_{out} vs. V_{in}

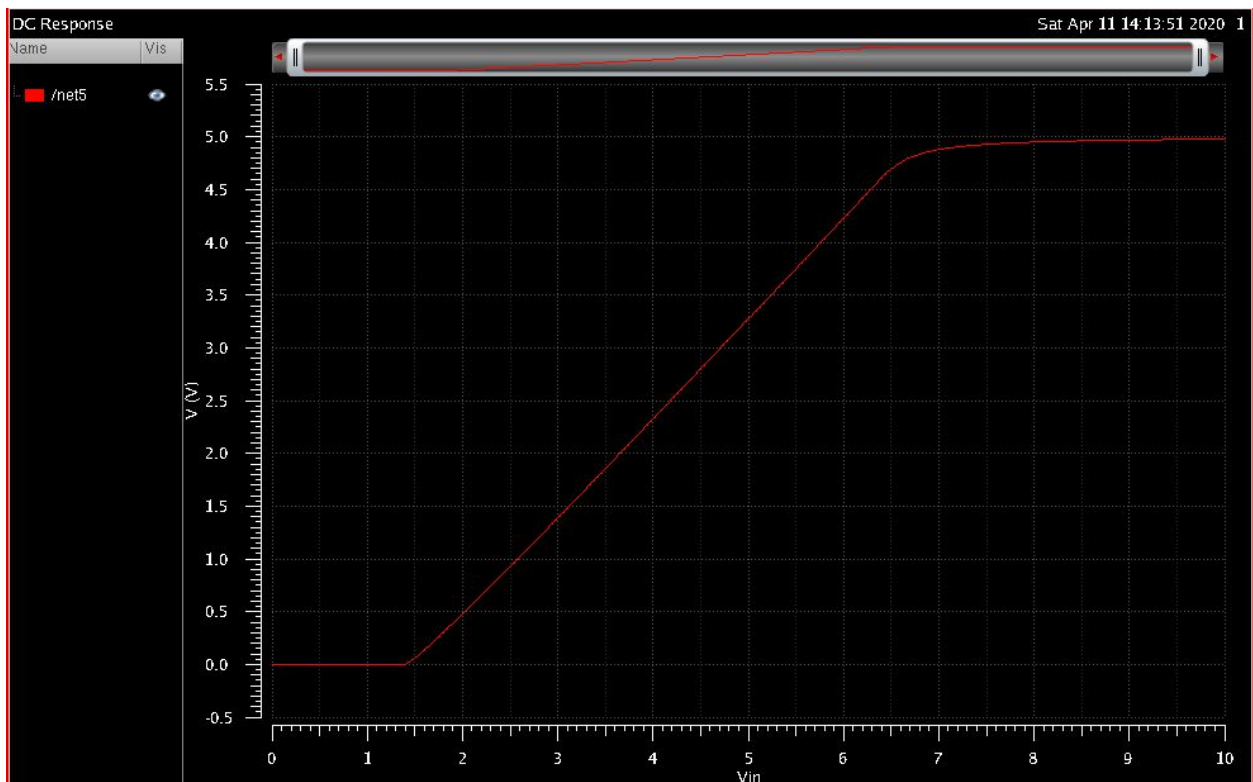

- $V_{in} = V_{in(eq1)}: \frac{6.33V - 1.44V}{2} = 2.445V$
- Region of operation (from bottom to top of graph): 1) cutoff, 2) saturation, 3) triode

B.

DC Operating Point Analysis

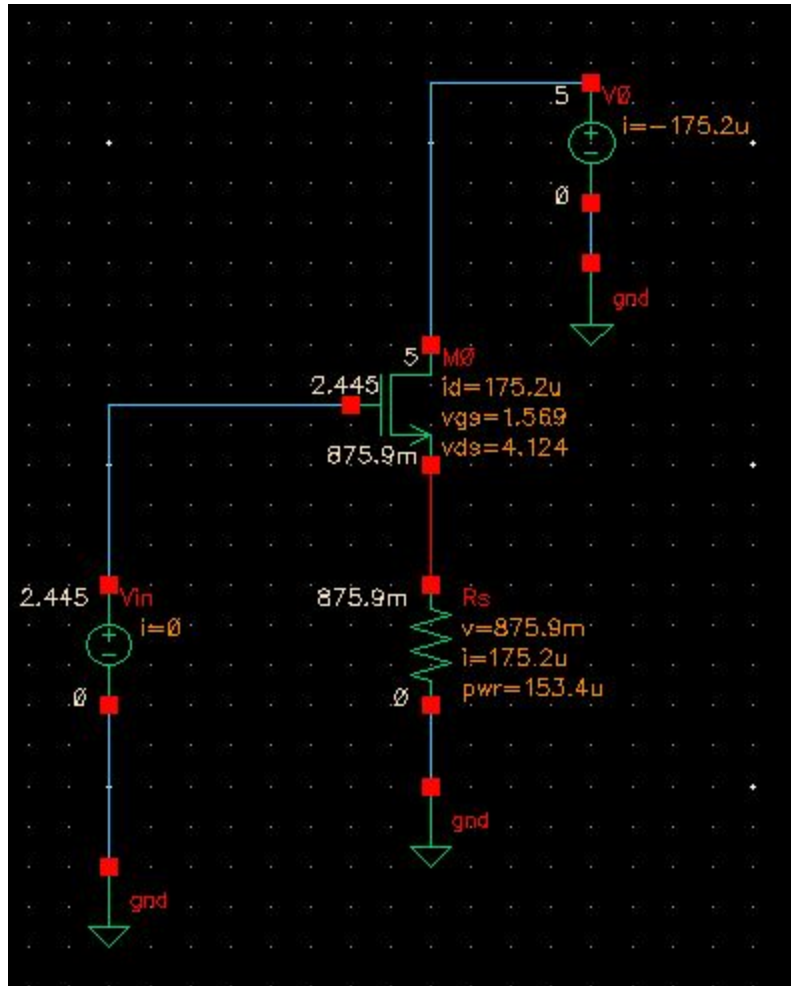

C.

Calculations

Small signal parameters from simulation:

- $g_m = 2.072n$
- $r_o = 1.11 M\Omega$

Calculated small signal parameters

- $g_m = \frac{2I_{ds}}{V_{gs} - V_t} = 2.061n$
 - $I_{ds} = k'/2(W/L)(V_{gs} - V_t)^2 \Rightarrow 175.2\mu = 0.6m/2(200\mu/10\mu)(V_{gs} - V_t)^2$
 - $V_{gs} = \sqrt{(175.2\mu/6m)} + 1.4 = 1.57V$

- $r_o = \frac{1}{\lambda I_{ds}} = 1/(0.005)(175.2\mu) = 1.14 \text{ M}\Omega$

Percent error:

- $g_m \text{ \% error} = 2.072\text{n} - 2.061\text{n} / 2.072\text{n} * 100\% = 0.53\%$
- $r_o \text{ \% error} = |1.11\text{M}\Omega - 1.14\text{M}\Omega| / 1.11\text{M}\Omega * 100\% = 2.7\%$

D.

Comparing AC and DC components of V_{in} and V_{out}



- DC input level: 2.445V
- DC output level: 0.876V
- Amplitude V_{in} : 20mV
- Amplitude V_{out} : 885 mV - 866 mV = 19mV
- Gain = $\text{Amp}_{V_{out}} / \text{Amp}_{V_{in}} = 20/19 = 1.05$
- DC and AC output levels decrease when adding a sine wave input and the gain is small.

E.

Increase $V_{in}(eq1)$ by 10mV

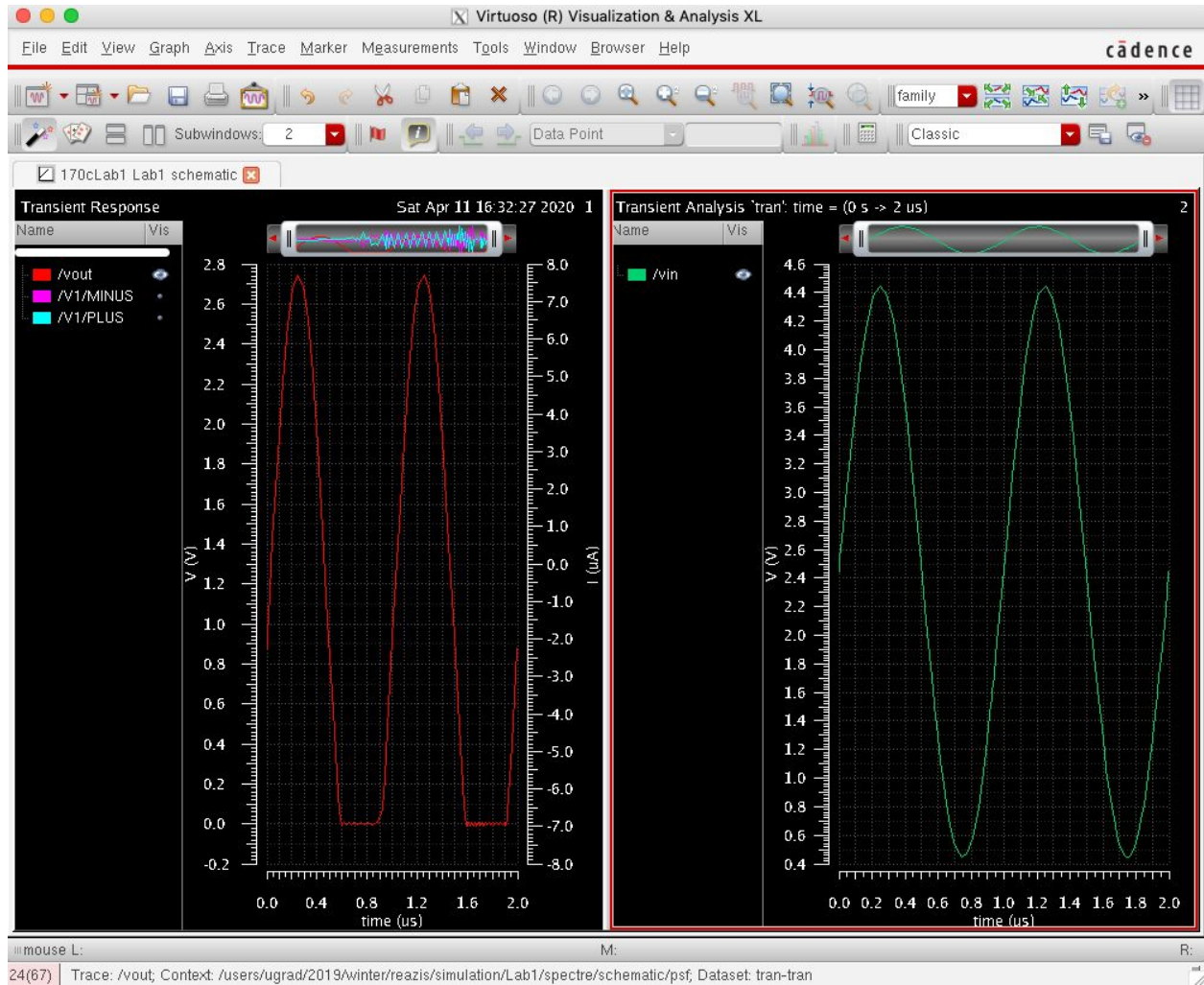


Fig. 1

- Since this is a buffer circuit, increasing V_{in} by 10mV will have no effect on the amplitude. However, increasing the amplitude from 10mV to 2V, which would be the maximum value, shows that V_{out} will start to clip (Fig.1). On the other hand, if V_{in} is increased significantly the output does not clip but the input does at around 14.4V (Fig. 2).


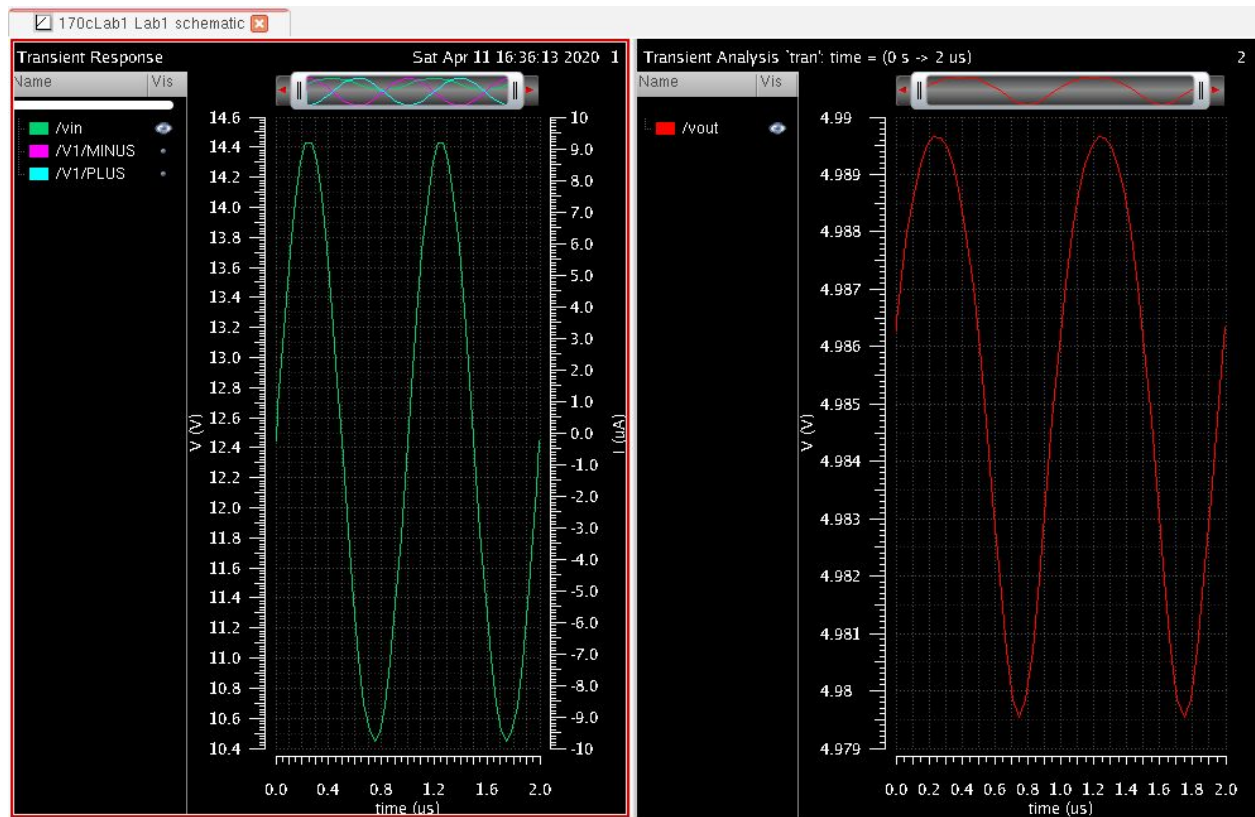


Fig.2

Problem 2

A.


V_{out} vs. V_{in}

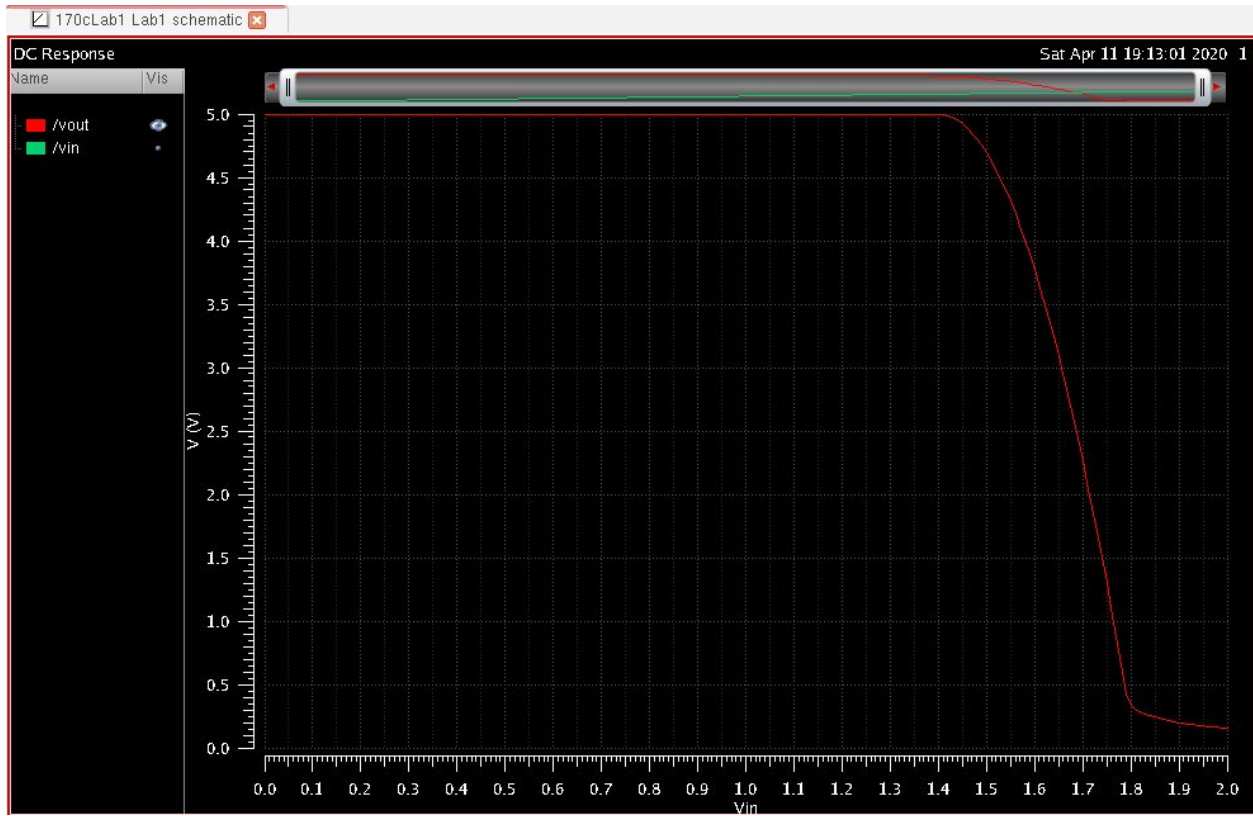

- Region of operation (from top to bottom of graph): 1) cutoff, 2) saturation, 3) triode


B.

$$V_{in} = V_{in(eq2)}$$

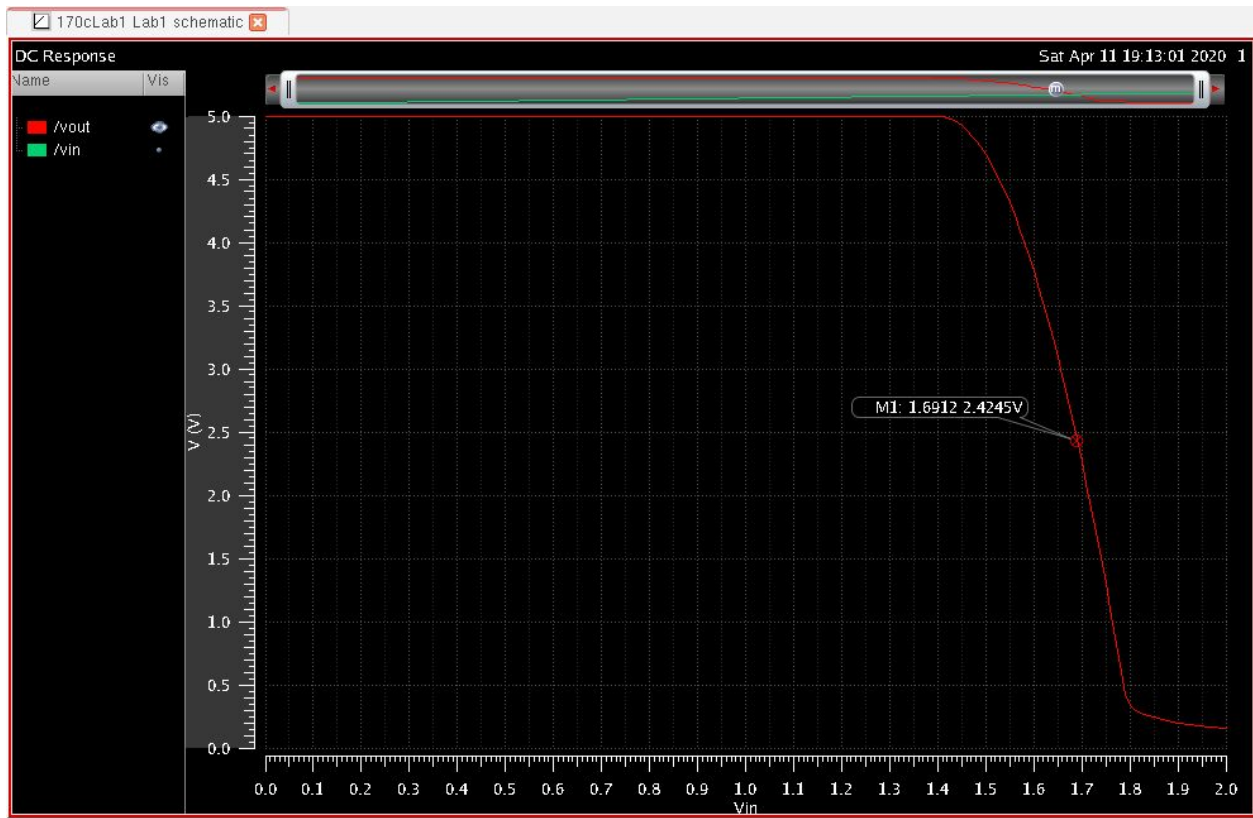

- $V_{out} = 1.69V$
- $V_{in} = V_{in(eq2)}: \frac{5V - 0.155V}{2} = 2.422V$

DC Operating Point Analysis

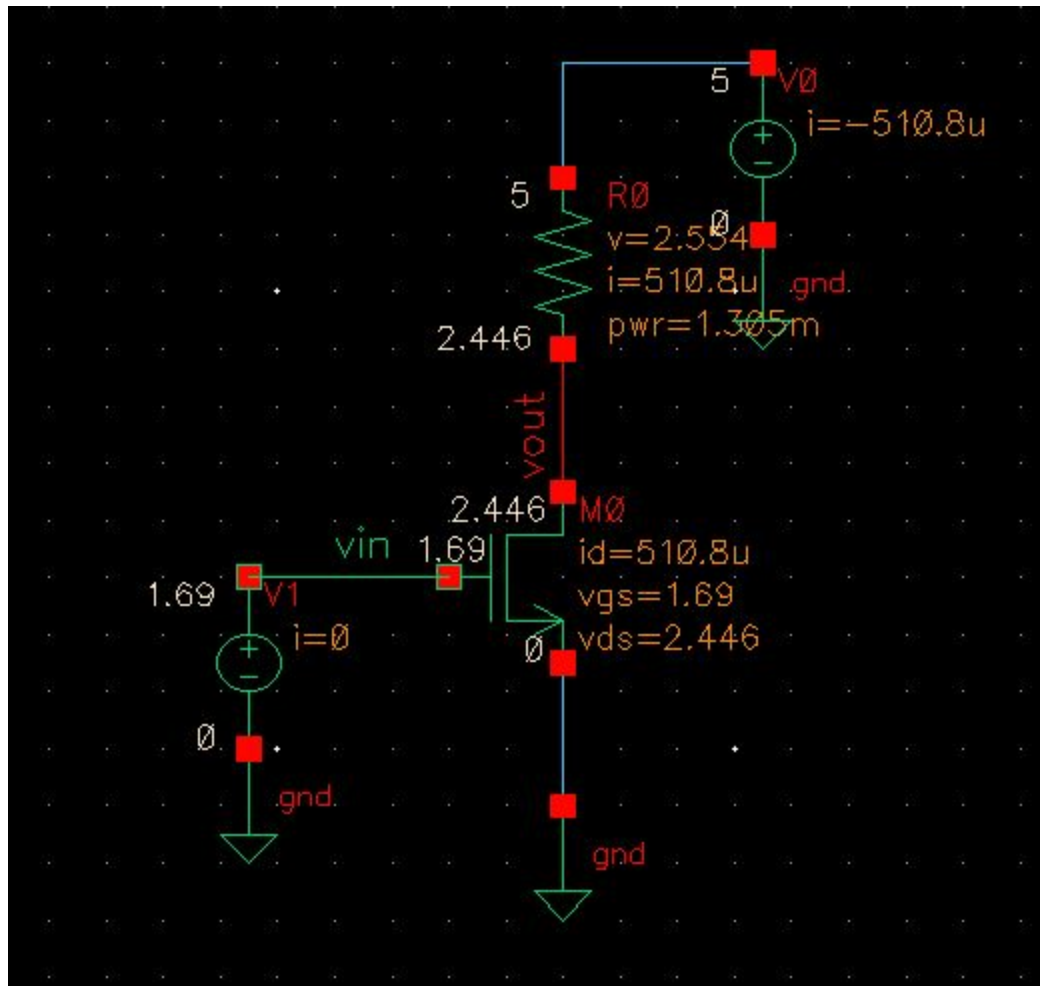

- The transistor is operating in saturation mode since $V_{ds} \geq V_{gs} - V_t$.
 - $2.446V \geq 1.69V - 1.4V$

C.

Calculations

Small signal parameters from simulation:

- $g_m = 3.523m$
- $r_o = 0.386 M\Omega$

Calculated small signal parameters

- $g_m = \frac{2I_{ds}}{V_{gs} - V_t} = 3.517m$
 - $I_{ds} = k'/2(W/L)(V_{gs} - V_t)^2 \Rightarrow 510.8\mu = 0.6m/2(200\mu/10\mu)(V_{gs} - V_t)^2$
 - $V_{gs} = \sqrt{(510.8\mu/6m)} + 1.4 = 1.69V$

- $r_o = \frac{1}{\lambda I_{Ds}} = 1/(0.005)(510.8\mu A) = 0.392 \text{ M}\Omega$

Percent error:

- gm % error = $3.523\text{n} - 3.517\text{n} / 3.523\text{n} * 100\% = 0.17\%$
- r_o % error = $|0.386\text{M}\Omega - 0.392\text{M}\Omega| / 0.386\text{M}\Omega * 100\% = 1.5\%$

D.

Gain for common source circuit

- $A = g_m * (R_d \parallel r_o)$, Accepted gain: 17.3
- Slope $(5 - 0.311) / (1.8 - 1.43) = 12.64$
- Calculated gain: $A = 3.523\text{m} * (4.9\text{k}) = \underline{17.26}$
- $r_o = 1/g_{ds} = 1/2.586\mu = \underline{386\text{k}}$

Gain percent error:

$$17.3 - 17.26 / 17.3 * 100\% = \underline{0.23\%}$$

E.

Comparing AC and DC components of V_{in} and V_{out}



- DC input level: 1.69V
- DC output level: 2.45V
- Amplitude_Vin $1.691 - 1.689 = 2\text{mV}$
- Amplitude_Vout $2.4631 - 2.4284 = 34.7\text{mV}$
- Gain = $\text{Amp_Vout} / \text{Amp_Vin} = 34.7/2 = 17.35$
- DC and AC output levels increase when adding a sine wave input and the gain is high.

F.

Increase Vin(eq2) by 10mV





- Increasing $V_{in}(\text{eq2})$ by 10 mV increases the amplitude of the output to 347 mV.

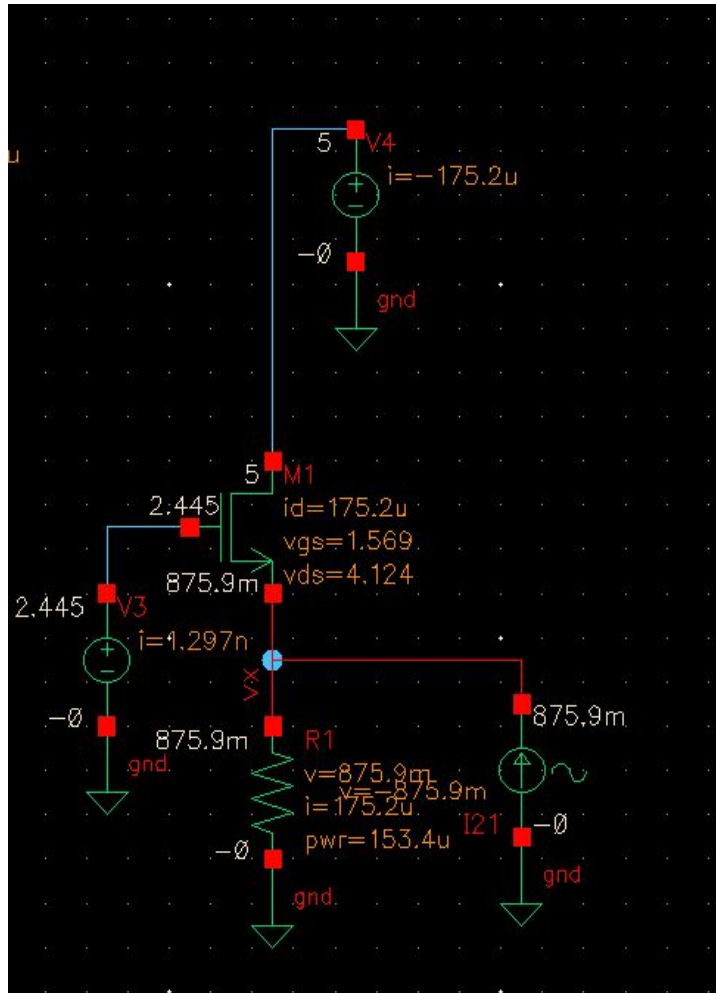Problem 3

A.

Calculate R_{out} for a common source circuit




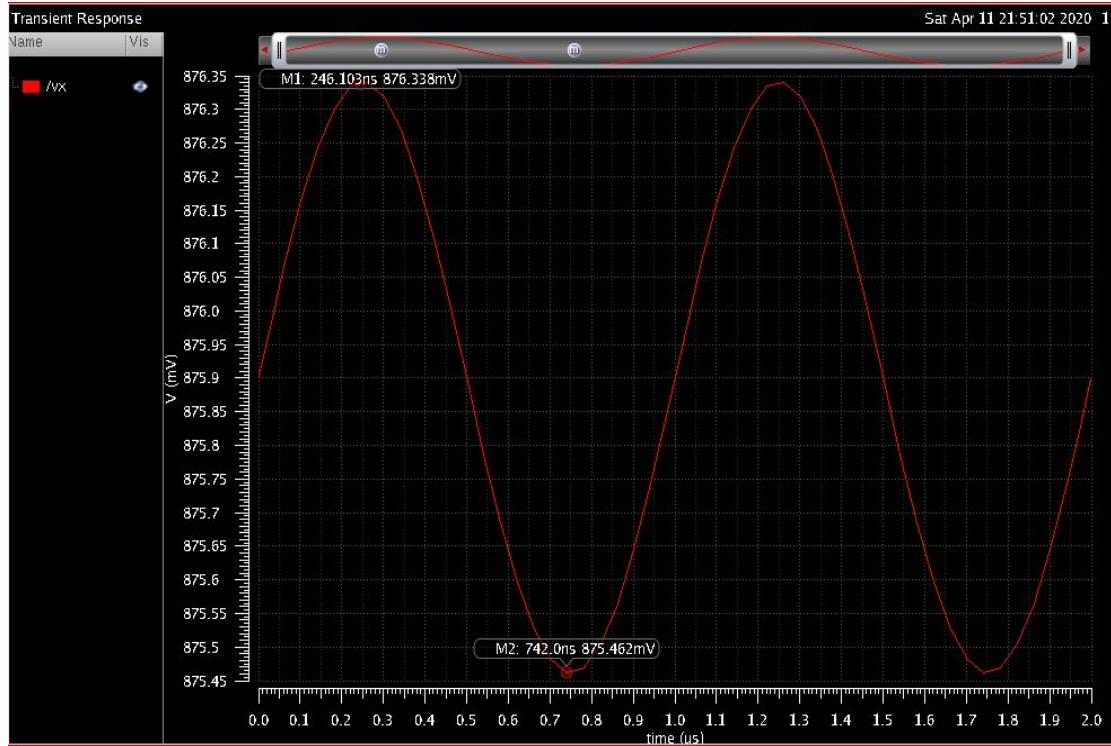


- $R_{out} = \text{Amp_vx} / \text{Amp_ix}$
- $\text{Amp_Vx} = 876.3 - 875.4 \text{ mV} = 0.9 \text{ mV} = 900 \mu\text{V}$
- $\text{Amp_Ix} = 2 \mu\text{A}$
- $R_{out} = 900 \mu\text{V} / 2 \mu\text{A} = \underline{450 \text{ ohm}}$

B.

Calculate R_{out} for common drain

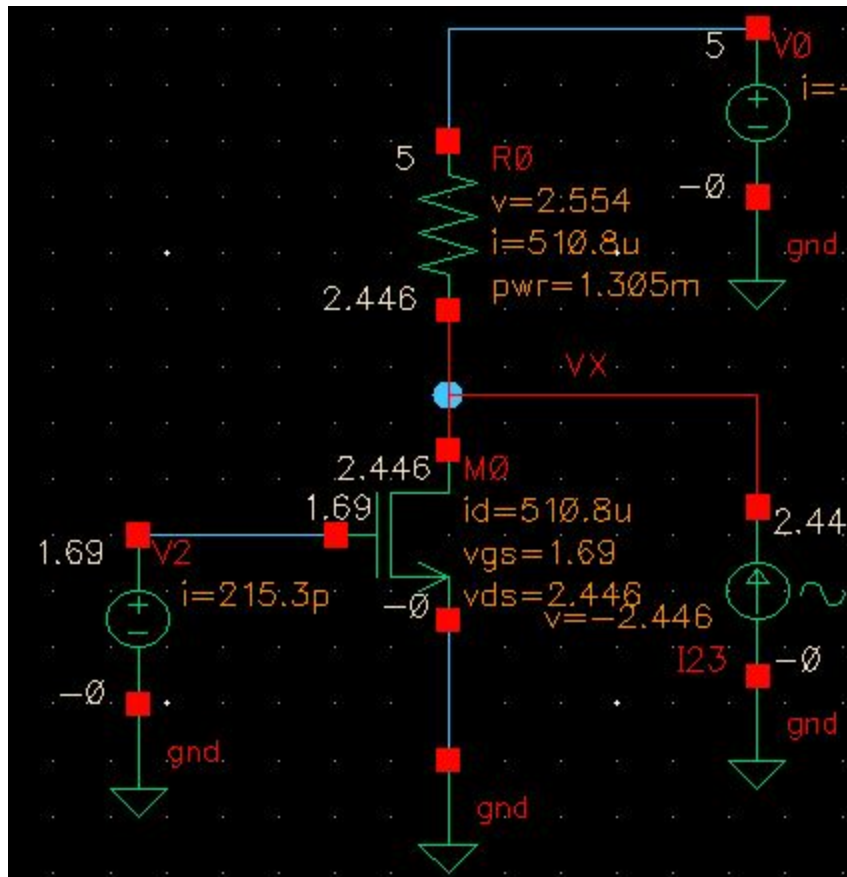

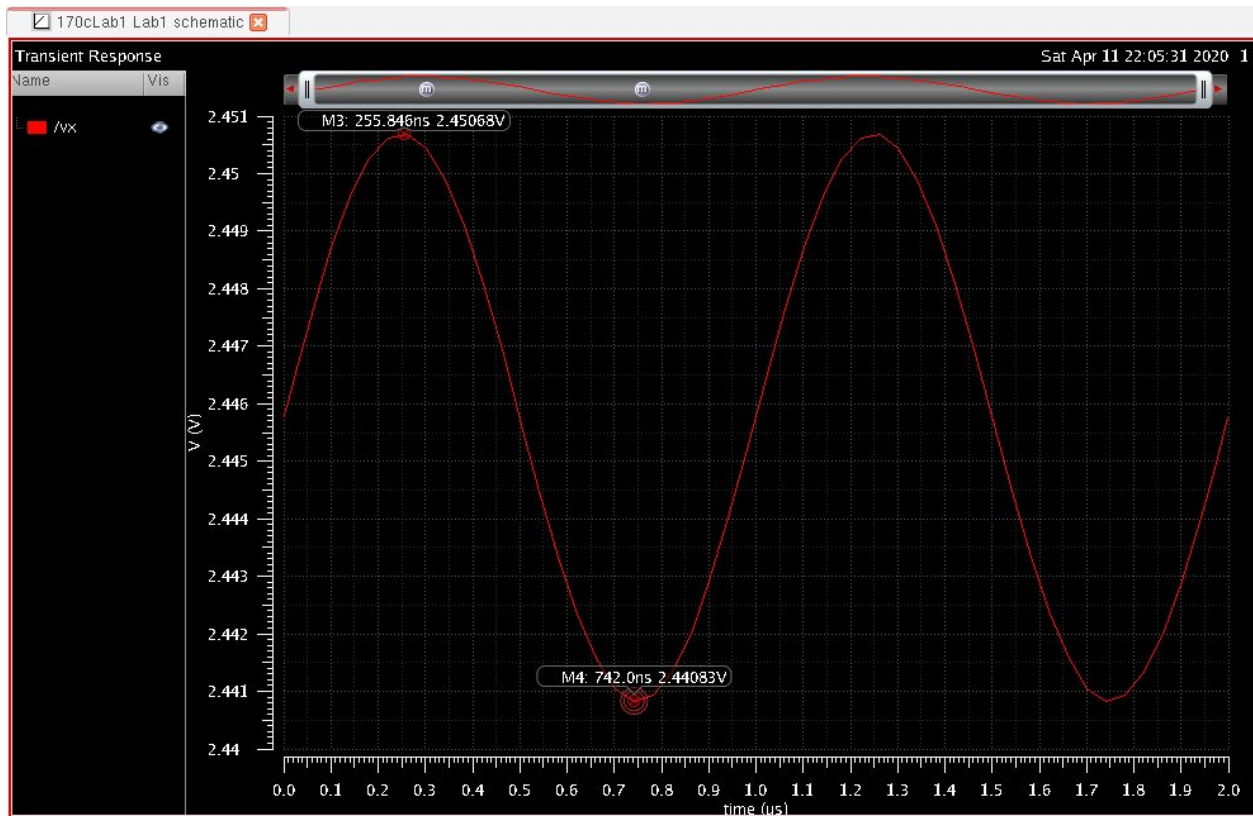



- $R_{out} = \text{Amp } v_x / \text{Amp } i_x$
- $\text{Amp } V_x = 2.45\text{V} - 2.44\text{V} = 0.01\text{V} = 10\text{mV}$
- $\text{Amp } I_x = 2\mu\text{A}$
- $R_{out} = 10\text{mV} / 2\mu\text{A} = \underline{5\text{k}}$

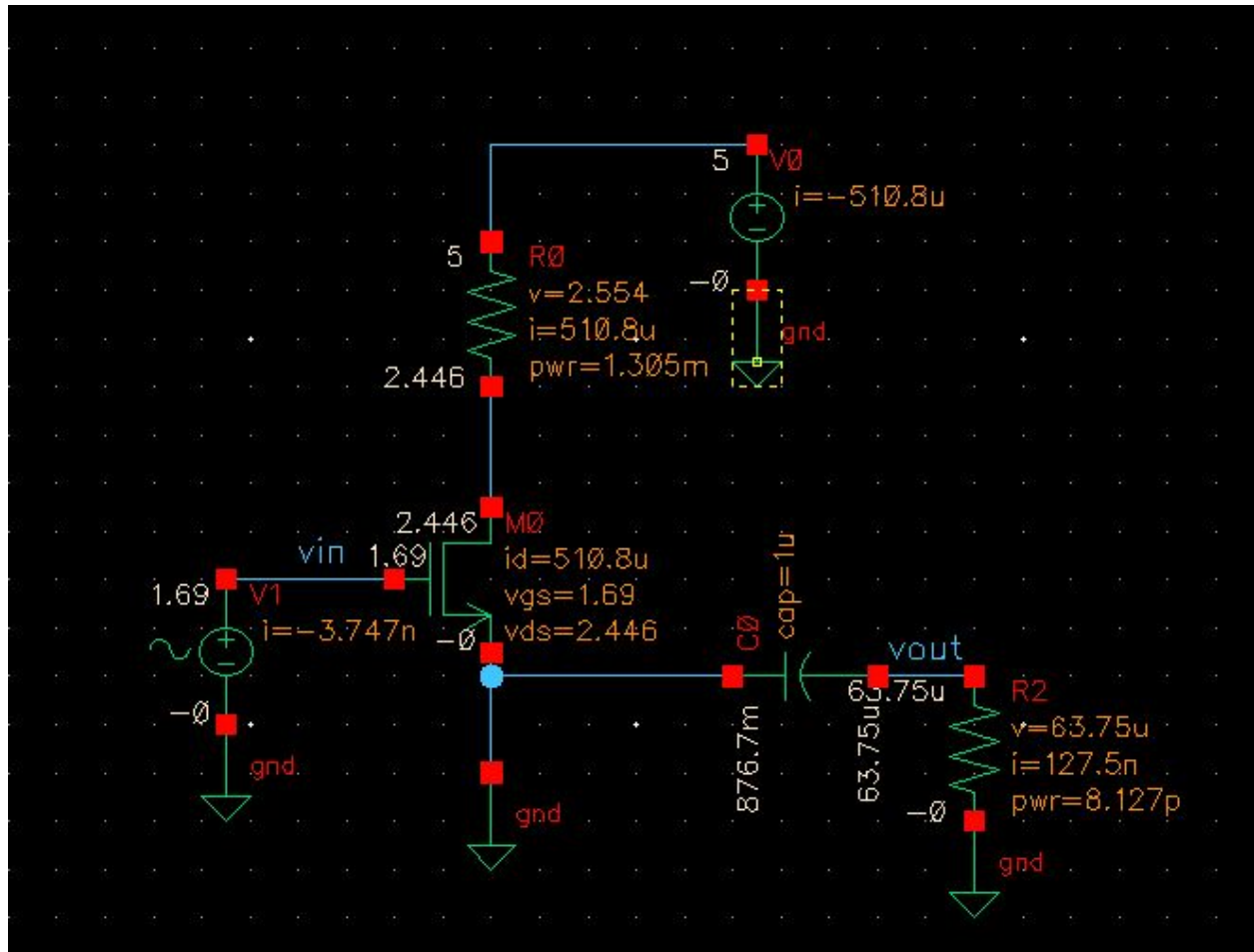Problem 4

A.

Small-signal gain V_{out}/V_{in} for one stage amplifier





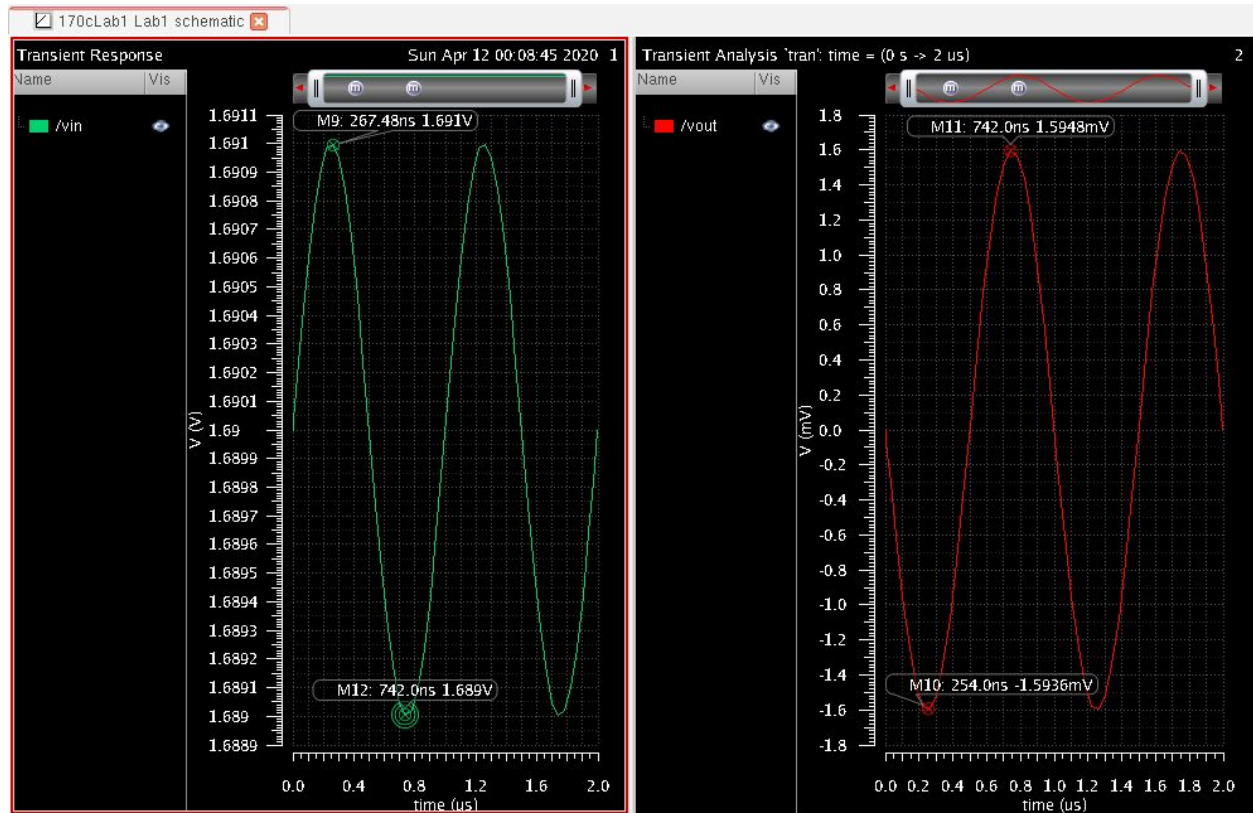

- $A = g_m * (R_d \parallel r_o \parallel R_L) = g_m * (R_d \parallel R_L)$. Since r_o is large it goes to 0.
- $A = g_m * (R_L)$. Since R_d is a lot smaller than R_L , it goes to 0. This will decrease the gain.
- $Amp_vout = 1.59mV$
- $Amp_vin = 2mV$
- DC output level is 0 because we are looking at V_{out} after the capacitor.
- $Gain = Amp_vout / Amp_vin = 0.795$. Small!

B.

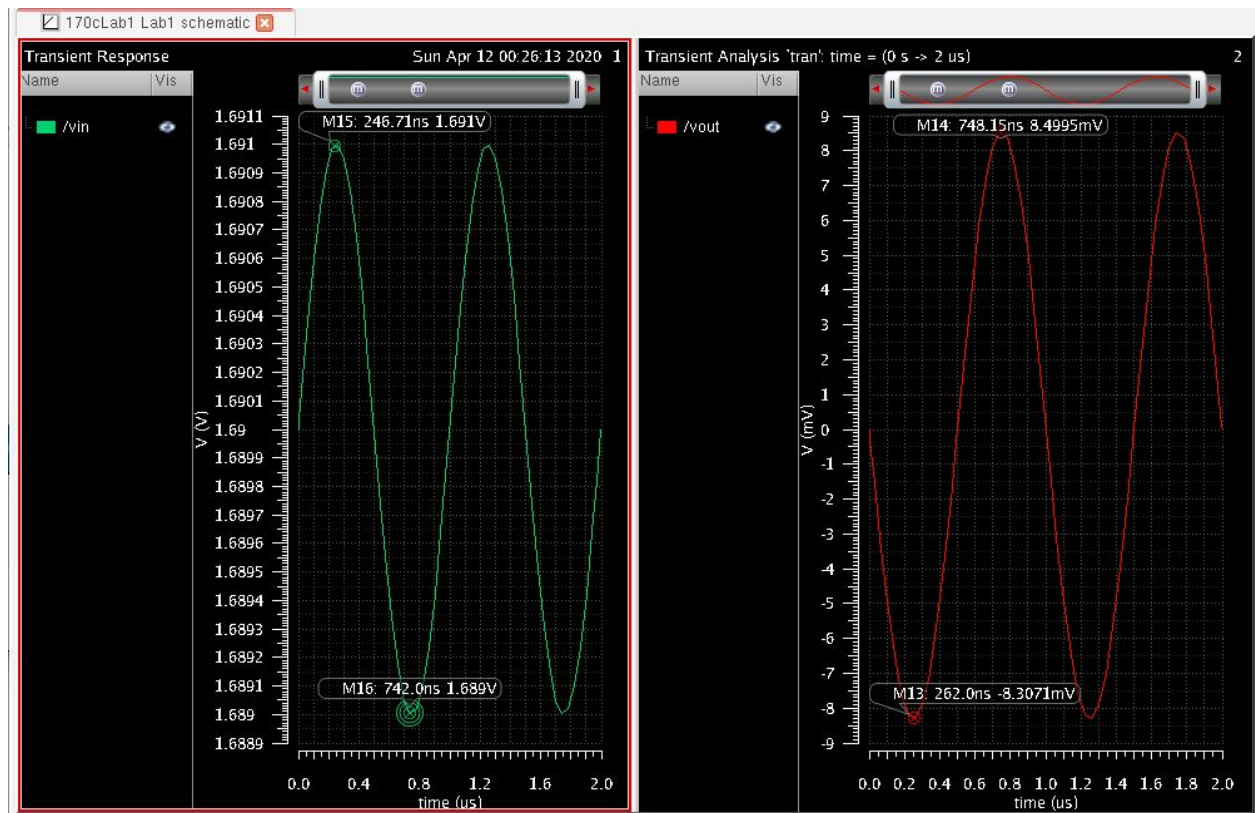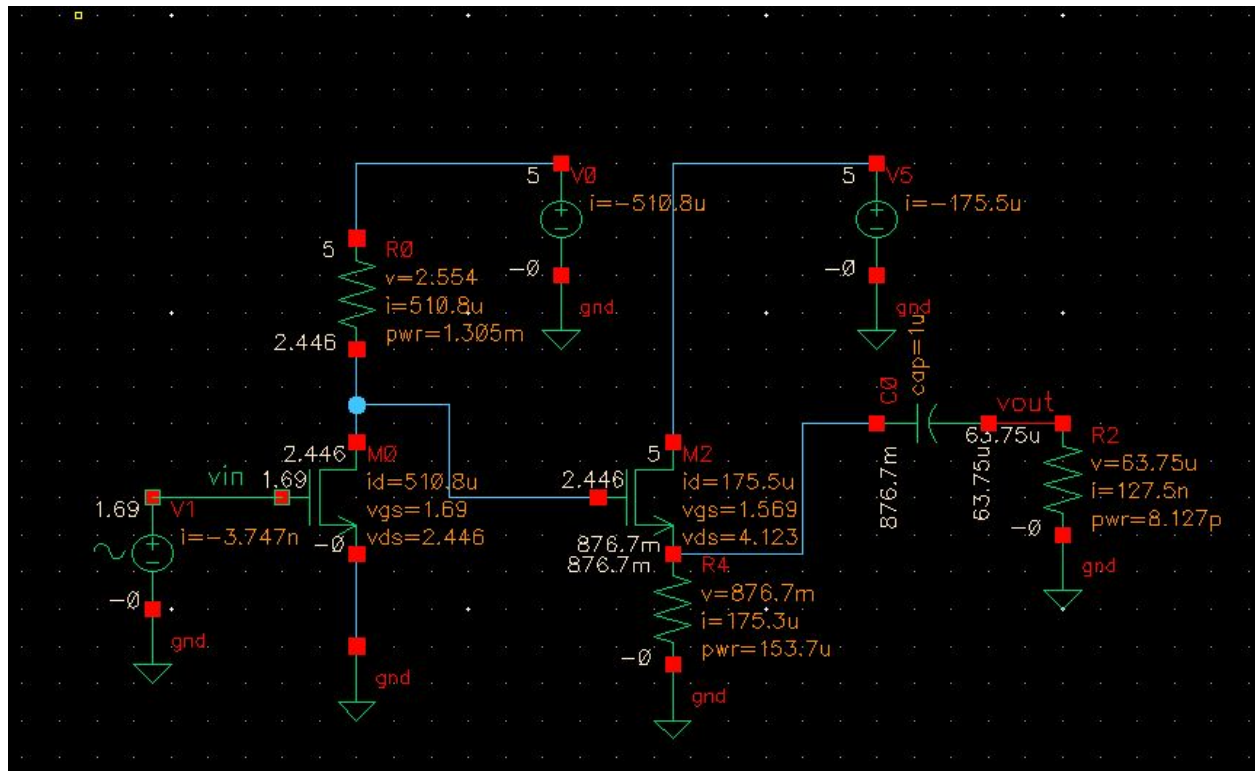Small signal gain V_{out}/V_{in} for two stage amplifier



- $\text{Gain} = A_1 * A_2$
- $A_1 = g_m * R_d$
- $A_2 = (R_s || R_I) / (1/g_m + R_s || R_I)$
- $\text{Gain} = g_m * R_d$ <- expecting higher gain
- $A_{\text{vout}} = 8.4\text{mV}$
- $A_{\text{vin}} = 2\text{mV}$
- $\text{Gain} = A_{\text{vout}}/A_{\text{vin}} = 4.2$ which is a lot higher than previous the one-stage amplifier

Conclusion

The simulations given produced the results as expected. In the common drain and common source circuit, the correct plots along with the calculations for $V_{in}(\text{eq1})$ and $V_{in}(\text{eq2})$, g_m , and r_o were determined. The percent error between the actual and calculated values for g_m and r_o were small. In the circuits, R_{out} was calculated by putting a current source on the source and drain, respectively. To consider the effects of loading on the common source and common drain circuit, a capacitor was connected to the circuit. In the circuit with one transistor, the gain is small but when there are two transistors connected together, the gain is a lot higher thus making the circuit more robust.